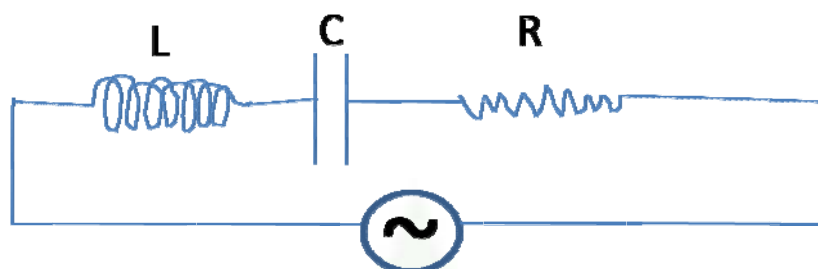




LCR Circuit

L-C-R circuit:



The impedance of the circuit

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

The emf may lead or lag the current depends on the values of ω , L & C

(1) If $\omega L > \frac{1}{\omega C}$ then emf leads the current by phase angle ϕ

$$\text{where } \tan \phi = \frac{\left(\omega L - \frac{1}{\omega C}\right)}{R}$$

(2) If $\omega L < \frac{1}{\omega C}$ the emf lags the current by a phase angle ϕ

$$\text{where } \tan \phi = \frac{\left(\frac{1}{\omega C} - \omega L\right)}{R}$$